

Solutions to Tutorial Sheet -7

I E C I O G

Q1. Derive expression for ripple factor of the unregulated power supply using capacitor filter shown in Fig. Q1 below.

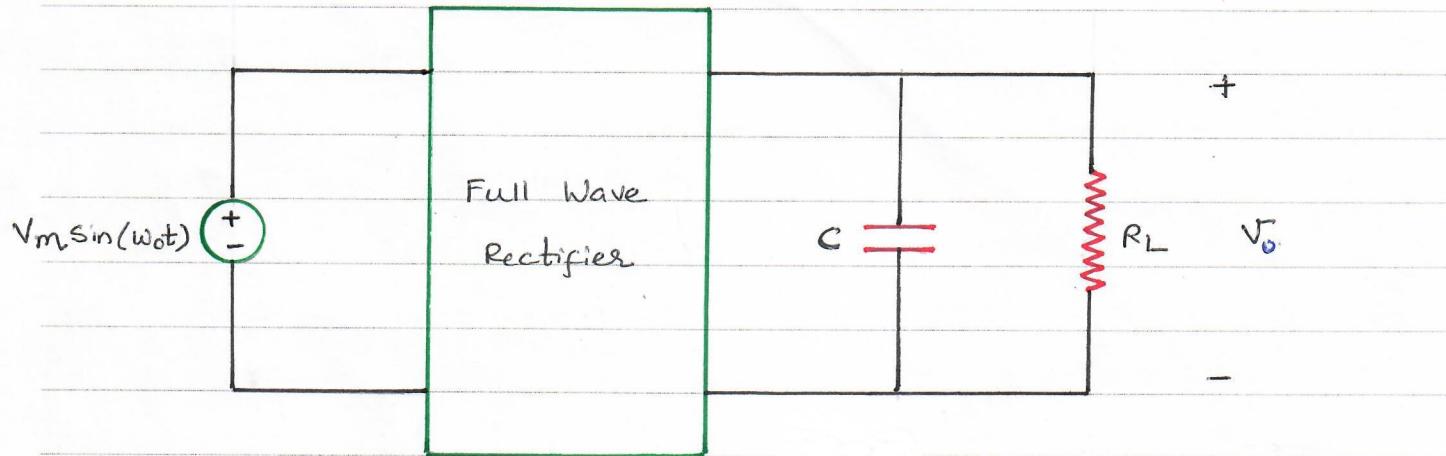


Fig. Q1


Assume the time constant  $R_L C$  is much greater than the time period of the source voltage.

Sol.


$$\omega_0 = 2\pi f$$

The output waveform will be as shown below.
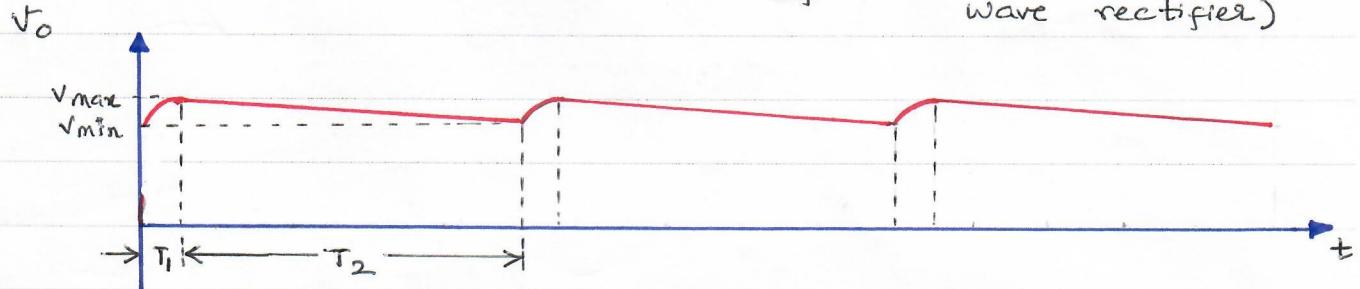
$$T = T_1 + T_2 = \frac{1}{2f} \quad (\text{since rectifier is a full wave rectifier})$$



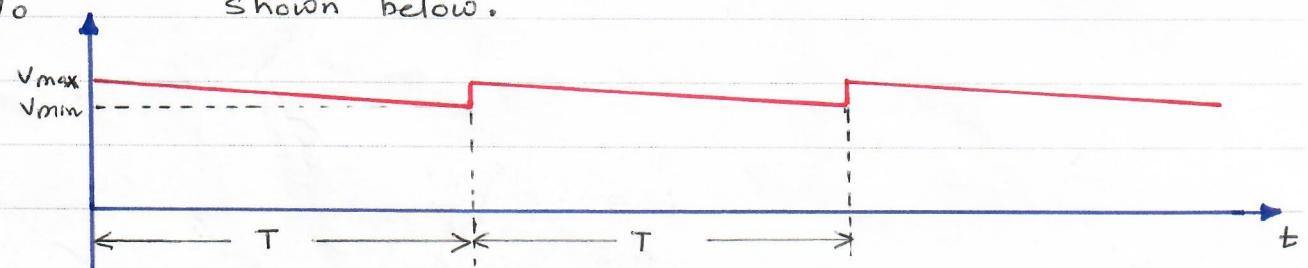$T = T_1 + T_2$  The above waveform can be approximated to waveform shown below.



$$R_L C \gg T$$

$$V_{\min} = V_{\max} e^{-T/R_L C}$$

$$= V_{\max} \left( 1 - \frac{T}{R_L C} + \frac{T^2}{2R_L^2 C^2} - \dots \right)$$

$$\approx V_{\max} \left( 1 - \frac{T}{R_L C} \right) \quad \because R_L C \gg T$$

Ripple factor =  $\frac{\text{RMS value of ripple voltage}}{\text{DC value of the voltage}}$

$$V_{DC} = \frac{(V_{\max} + V_{\min})}{2} = \frac{1}{2} \left[ V_{\max} + V_{\max} \left( 1 - \frac{T}{R_L C} \right) \right]$$

$$= \frac{1}{2} \left[ V_{\max} + V_{\max} - V_{\max} \frac{T}{R_L C} \right]$$

$$= \frac{1}{2} \left[ 2V_{\max} - V_{\max} \frac{T}{R_L C} \right]$$

$$= V_{\max} \left( 1 - \frac{T}{2R_L C} \right)$$

$$\text{Peak-to-peak to ripple voltage} = V_{\max} - V_{\min} = V_{P-P}$$

$$= V_{\max} - V_{\max} \left( 1 - \frac{T}{R_L C} \right)$$

$$= V_{\max} \frac{T}{R_L C} = V_{P-P}$$

$$\text{RMS value of ripple voltage} = \frac{V_{P-P}}{\sqrt{3}} = \frac{V_{\max} T}{\sqrt{3} R_L C}$$


$$\therefore \gamma = \frac{V_{\max} T}{\sqrt{3} R_L C}$$

$$\therefore \gamma = \frac{V_{\max} \left( 1 - \frac{T}{R_L C} \right)}{\sqrt{3} R_L C} = \frac{T}{\sqrt{3} R_L C \left( 1 - \frac{T}{R_L C} \right)} = \frac{T}{\sqrt{3} (R_L C - T)}$$


$$\approx \frac{T}{2\sqrt{3} R_L C} = \frac{1}{4\sqrt{3} f R_L C}$$

$$\therefore T = \frac{1}{2f}$$

## 2nd method

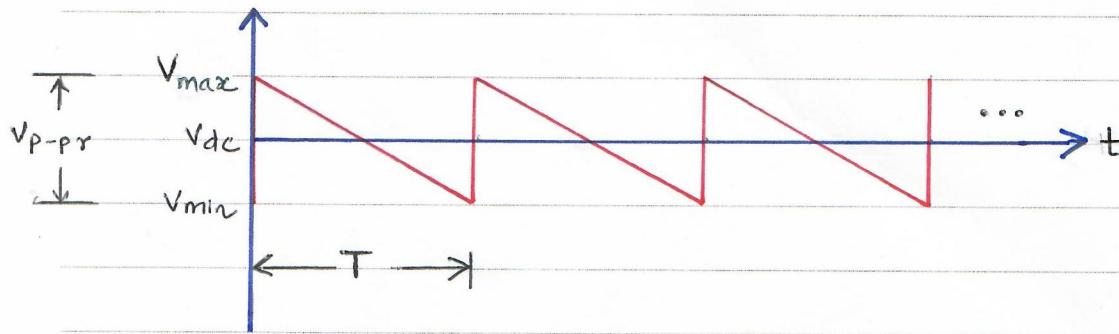

RMS value of ripple voltage

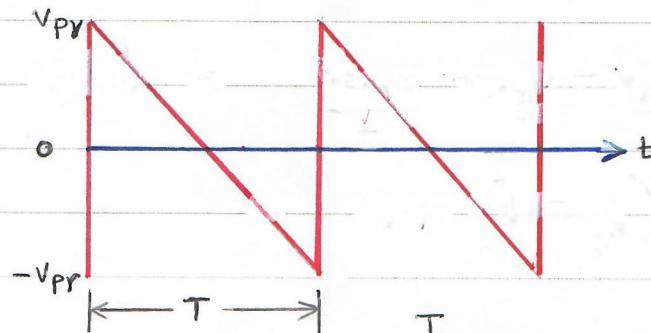

$$V_r(t) = V_{pr} + \frac{(-V_{pr} - V_{pr})t}{T}$$

$$= V_{pr} \left( 1 - \frac{2t}{T} \right)$$

$$V_r^2(RMS) = \frac{1}{T} \int_0^T \left[ V_{pr} \left( 1 - \frac{2t}{T} \right) \right]^2 dt$$

$$= \frac{V_{pr}^2}{T} \int_0^T \left( 1 + 4\frac{t^2}{T^2} - \frac{4t}{T} \right) dt$$

$$= \frac{V_{pr}^2}{T} \left[ t + \frac{4t^3}{3T^2} - \frac{4t^2}{2T} \right]$$

$$= \frac{V_{pr}^2}{3}$$

$$\Rightarrow V_r(RMS) = \frac{V_{pr}}{\sqrt{3}} = \frac{V_{pr}}{\sqrt{3}} = \frac{V_{p-pr}}{2\sqrt{3}}$$

$V_{p-pr} = 2V_{pr}$

$$V_{min} = V_{max} e^{-T/R_{LC}} \approx V_{max} \left( 1 - \frac{T}{R_{LC}} \right)$$

$$V_{dc} = \frac{V_{max} + V_{min}}{2} = \frac{V_{max}}{2} + \frac{V_{max}}{2} \left( 1 - \frac{T}{R_{LC}} \right) = V_{max} \left( 1 - \frac{T}{2R_{LC}} \right)$$

$$V_{P-pr} = V_{max} - V_{min} = V_{max} - V_{max} \left(1 - \frac{T}{R_L C}\right)$$

$$= \frac{V_{max} T}{R_L C}$$

$$\therefore V_r(\text{rms}) = \frac{V_{max} T}{2\sqrt{3} R_L C}$$

$$V_{dc} = V_{max} \left(1 - \frac{T}{2R_L C}\right)$$

$$r = \frac{V_r(\text{rms})}{V_{dc}} = \frac{\frac{V_{max} T}{2\sqrt{3} R_L C}}{V_{max} \left(1 - \frac{T}{2R_L C}\right)}$$

$$= \frac{T}{2\sqrt{3} R_L C \left(1 - \frac{T}{2R_L C}\right)}$$


$$= \frac{T}{2\sqrt{3} (R_L C - \frac{T}{2}) R_L C}$$

$R_L C \gg T$

$$\approx \frac{T}{2\sqrt{3} R_L C} = \frac{1}{4\sqrt{3} f R_L C}$$

$$\therefore T = \frac{1}{2f}$$

### 3rd Method

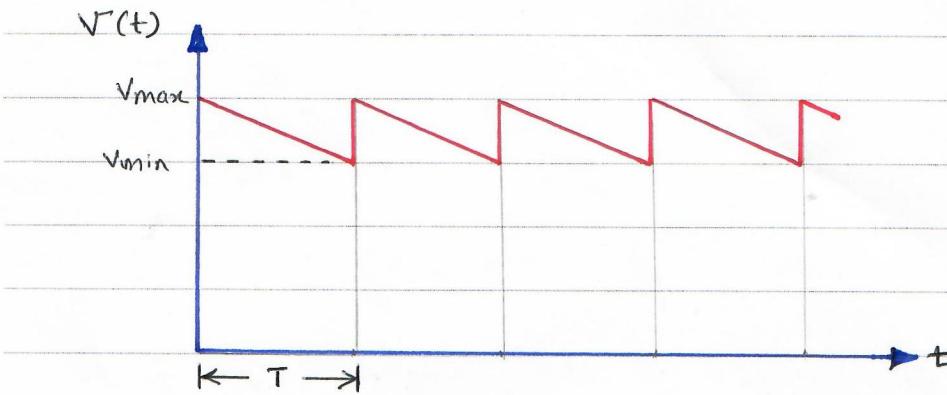

$$R_L C \gg T$$

$$V_{\text{min}} = V_{\text{max}} e^{-T/R_C} \approx V_{\text{max}} \left( 1 - \frac{T}{R_C} \right)$$

$$\text{Ripple factor } \gamma = \sqrt{\frac{V_{\text{rms}}^2 - V_{\text{dc}}^2}{V_{\text{dc}}^2}}$$

$$\begin{aligned} V_{\text{dc}} &= \frac{V_{\text{max}} + V_{\text{min}}}{2} = \frac{1}{2} \left[ V_{\text{max}} + V_{\text{max}} \left( 1 - \frac{T}{R_C} \right) \right] \\ &= \frac{1}{2} V_{\text{max}} \left( 1 + 1 - \frac{T}{R_C} \right) \end{aligned}$$

$$\Rightarrow V_{\text{dc}} = V_{\text{max}} \left( 1 - \frac{T}{2R_C} \right)$$

$$V_{\text{rms}}^2 = \frac{1}{T} \int_0^T V(t)^2 dt$$

$$\text{where } V(t) = V_{\text{max}} + \frac{(V_{\text{min}} - V_{\text{max}})}{T} t \quad 0 < t < T$$

$$= V_{\text{max}} \left( 1 - \frac{t}{T} \right) + \frac{V_{\text{min}} t}{T}$$

$$= V_{\text{max}} \left( 1 - \frac{t}{T} \right) + V_{\text{max}} \left( 1 - \frac{T}{R_C} \right) \frac{t}{T}$$

$$= V_{\text{max}} \left[ \left( 1 - \frac{t}{T} \right) + \left( 1 - \frac{T}{R_C} \right) \frac{t}{T} \right]$$

$$\Rightarrow V(t) = V_{\text{max}} \left( 1 - \frac{t}{R_C} \right)$$

$$V_{rms}^2 = \frac{1}{T} \int_0^T V(t)^2 dt = \frac{1}{T} \int_0^T V_{max}^2 \left(1 - \frac{t}{R_L C}\right)^2 dt$$

$$= \frac{V_{max}^2}{T} \int_0^T \left(1 + \frac{t^2}{R_L^2 C^2} - \frac{2t}{R_L C}\right) dt$$

$$= \frac{V_{max}^2}{T} \left[ t + \frac{t^3}{3 R_L^2 C^2} - \frac{2t^2}{2 R_L C} \right]_0^T$$

$$= \frac{V_{max}^2}{T} \left[ T + \frac{T^3}{3 R_L^2 C^2} - \frac{T^2}{R_L C} \right]$$

$$= V_{max}^2 \left[ 1 + \frac{T^2}{3 R_L^2 C^2} - \frac{T}{R_L C} \right]$$

$V_r$  = Ripple voltage (RMS value)

$$V_r^2 = V_{rms}^2 - V_{dc}^2$$

$$\therefore V_r^2 = V_{max}^2 \left(1 + \frac{T^2}{3 R_L^2 C^2} - \frac{T}{R_L C}\right) - V_{max}^2 \underbrace{\left(1 - \frac{T}{2 R_L C}\right)^2}_{V_{dc}^2}$$

$$= V_{max}^2 \left(1 + \frac{T^2}{3 R_L^2 C^2} - \frac{T}{R_L C}\right) - V_{max}^2 \left(1 + \frac{T^2}{4 R_L^2 C^2} - \frac{T}{R_L C}\right)$$

$$= V_{max}^2 \left(1 + \frac{T^2}{3 R_L^2 C^2} - \frac{T}{R_L C} - 1 - \frac{T^2}{4 R_L^2 C^2} + \frac{T}{R_L C}\right)$$

$$= \frac{V_{max}^2 T^2}{12 R_L^2 C^2} = V_r^2$$

$$\therefore V_r = \frac{V_{max} T}{2 \sqrt{3} R_L C}$$

$$\text{Ripple factor} = \frac{V_r}{V_{dc}} = \frac{\frac{V_{max} T}{2 \sqrt{3} R_L C}}{V_{max} \left(1 - \frac{T}{2 R_L C}\right)} = \frac{V_{max} T}{2 \sqrt{3} R_L C} \times \frac{2 R_L C}{V_{max} (2 R_L C - T)}$$

$$\Rightarrow r = \frac{T}{\sqrt{3}(2R_L C - T)} \approx \frac{T}{2\sqrt{3}R_L C} \quad \because R_L C \gg T$$

$$\therefore r = \frac{T}{2\sqrt{3}R_L C} = \frac{1}{4\sqrt{3}R_L C f} \quad \therefore T = \frac{1}{2f}$$

$\therefore$    $r = \frac{1}{4\sqrt{3}f R_L C}$

(Q2) For the circuit shown in Fig. Q2, find the turns ratio of the transformer, the current rating of the diodes, and the value of  $C$ , so that the maximum value of voltage across the load should not exceed 15V and minimum value should not drop below 13V.

Take the charging time of capacitor is  $\frac{1}{10}$ th of the time period of the output waveform.

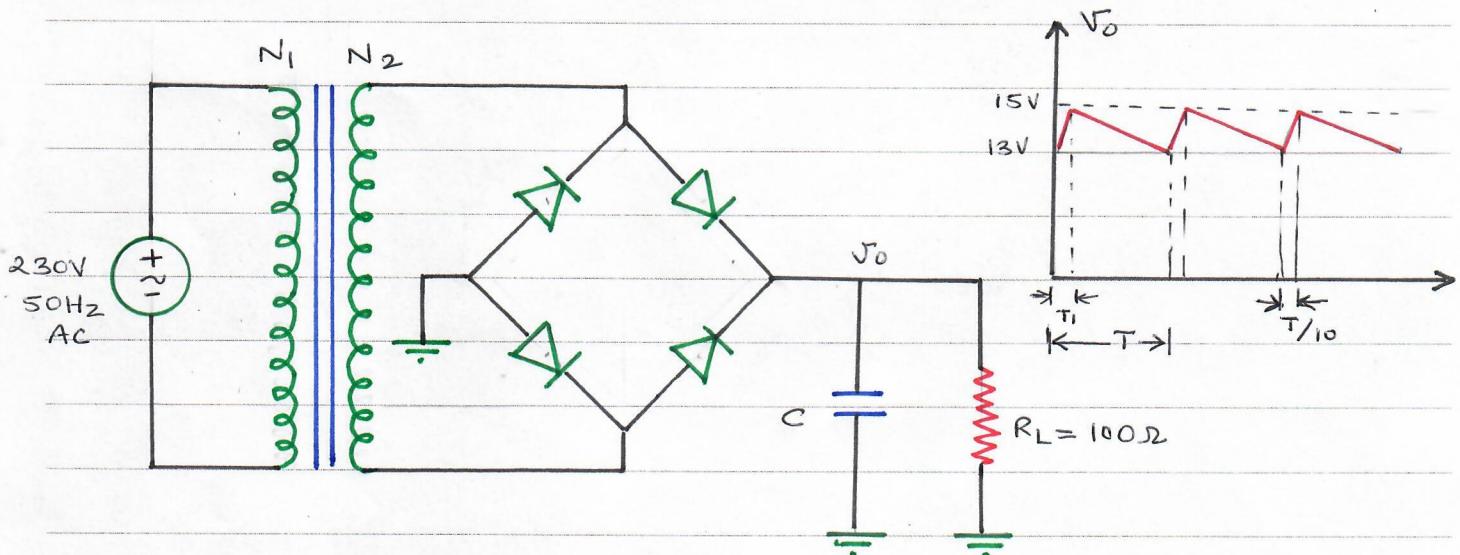


Fig. Q2

What will be the maximum current through diodes.

Sol.

Peak value of voltage across load = 15V = peak value of secondary voltage of transformer

Peak value of secondary voltage of the transformer = 15V

Peak value of primary voltage of the transformer =  $230\sqrt{2} = 325.27$  V

$$\frac{N_1}{N_2} = \frac{325.27}{15} = 21.685 \approx 22$$

$$V_o(\text{max}) = V_p = 15V$$

$$V_o(\text{min}) = 13V$$

Time period of the output waveform =  $\frac{1}{100} = 10 \text{ ms}$

$T_1$  = charging time ;  $T_2$  = discharging time

$$T_1 + T_2 = T$$

$$T_1 = \frac{T}{10} = 1 \text{ ms} \quad \Rightarrow \quad T_2 = 9 \text{ ms}$$

$$T_2 \approx T = 10 \text{ ms}$$

During the discharging of capacitor

$$V_o = V_{o(\max)} e^{-t/R_{LC}}$$

$$V_o \approx V_{o(\max)} \left( 1 - \frac{t}{R_{LC}} \right)$$

$$V_{o(\min)} \approx V_{o(\max)} \left( 1 - \frac{T_2}{R_{LC}} \right)$$

$$\Rightarrow C = \frac{V_{o(\max)} T_2}{R_L [V_{o(\max)} - V_{o(\min)}]}$$

$$= \frac{15 \times 9 \times 10^{-3}}{100 \times (15 - 13)} = \frac{15 \times 9 \times 10^{-3}}{200}$$

$$= \frac{15 \times 9 \times 10^{-5}}{2} \\ = 67.5 \times 10^{-5} \text{ F}$$

$$\Rightarrow C = 67.5 \mu\text{F}$$

$$R_{LC} = 100 \times 67.5 \times 10^{-6} = 67.5 \text{ ms} \gg T$$

$$\text{Maximum current through diodes} = C \frac{(V_{o(\max)} - V_{o(\min)})}{T_1}$$

$$i = C \frac{dV}{dt} = C \frac{\Delta V}{\Delta T} = C \frac{(V_{o(\max)} - V_{o(\min)})}{(T_1 - 0)} = 67.5 \times 10^{-5} \times \frac{(15 - 13)}{10^{-3}}$$

$$= 2 \times 67.5 \times 10^{-2}$$

$$= 1350 \text{ mA}$$

$$= 1.35 \text{ A}$$

The current rating of each diode should be more than

$$1.35 \text{ A}$$

$$I_D(\max) = 1.35 \text{ A}$$


Q3 Find the maximum and minimum value of  $R_s$  for a zener voltage regulator so as to maintain a constant DC voltage of 5V across load.

The zener diode ratings are

$$V_Z = 5V, I_{ZK} (\text{knee current}) = 0A, P_{Z(\text{max})} = 0.5W$$

The input voltage can vary from 7 to 10V and maximum load current is 20mA.

Sol.

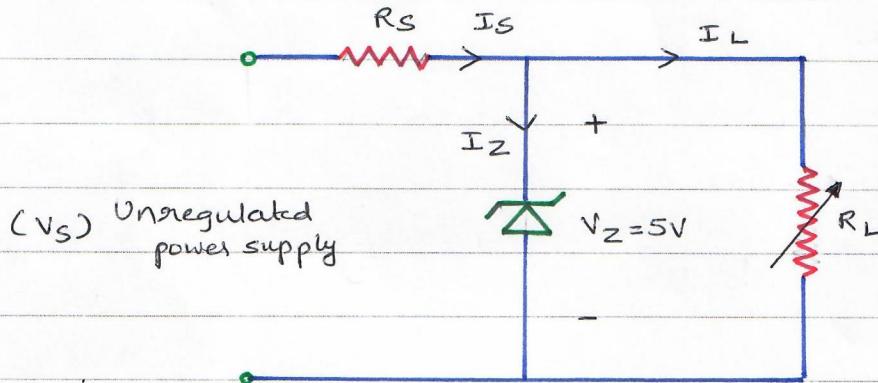

$$I_Z = I_S - I_L$$

$$\Rightarrow I_Z = \frac{V_S - V_Z}{R_s} - I_L$$

$$I_{Z(\text{max})} = \frac{V_{S(\text{max})} - V_Z}{R_{s(\text{min})}} - I_{L(\text{min})}$$

$$I_{Z(\text{min})} = \frac{V_{S(\text{min})} - V_Z}{R_{s(\text{max})}} - I_{L(\text{max})}$$

$$I_{Z(\text{min})} < I_Z < I_{Z(\text{max})}$$

$$I_{Z(\text{knee})} \leq I_Z \leq I \cdot \frac{P_{Z(\text{max})}}{V_Z}$$

$$V_{S(\text{max})} = 10V; V_{S(\text{min})} = 7V; I_{Z(\text{knee})} = 0A; I_{Z(\text{max})} = \frac{P_{Z(\text{max})}}{V_Z}$$

$$I_{L(\text{min})} = 0A; I_{L(\text{max})} = 20mA$$

$$= \frac{0.5}{5}$$

$$I_{Z(\text{max})} = \frac{10 - 5}{R_{s(\text{min})}} - 0 < 0.1 = 0.1A$$

$$\Rightarrow \frac{5}{R_{s(\text{min})}} - 0 < 0.1$$

$$\Rightarrow \frac{5}{R_{s(\text{min})}} < 0.1 \Rightarrow R_{s(\text{min})} > \frac{5}{0.1} = 50$$

$$\Rightarrow R_{s(\text{min})} > 50\Omega$$

$$I_{Z(\min)} = \frac{V_{S(\min)} - V_Z}{R_S(\max)} - I_{L(\max)} > I_{Z(\text{knee})}$$

$$\Rightarrow \frac{7 - 5}{R_S(\max)} - 0.02 > 0$$

$$\Rightarrow \frac{2}{R_S(\max)} > 0.02$$

$$\Rightarrow R_S(\max) < \frac{2}{0.02} = 100\Omega$$

∴  $R_S$  should lie between  $50\Omega$  to  $100\Omega$  for proper operation of zener regulator.

∴ We can choose  $R_S = 75\Omega$

(Q4) For the zener regulator shown in Fig. Q4, the input voltage can vary from 20 to 25V and the load resistance vary from  $500\Omega$  to  $2k\Omega$ .

The zener ratings are

$$V_Z = 3.3 \text{ V}; I_{Z(\text{knee})} = I_{Z(\text{min})} = 3 \text{ mA}; P_{Z(\text{max})} = 330 \text{ mW}$$

and maximum power  $P_Z = 330 \text{ mW}$

Determine the acceptable range of  $R_S$  for proper operation of the regulated power supply.

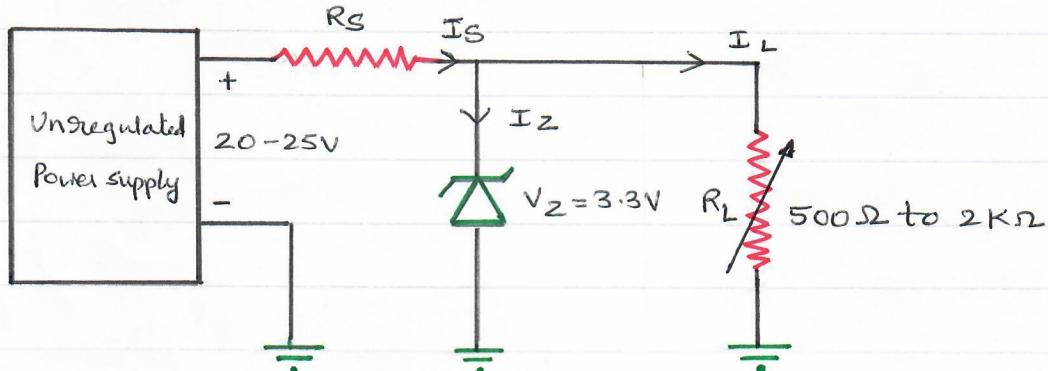


Fig. Q4

Sol. The current through the zener diode should be between  $I_{Z(\text{knee})}$  and  $I_{Z(\text{max})} = \frac{P_{Z(\text{max})}}{V_Z}$  for the

diode to be operated in the zener breakdown region to maintain constant voltage  $V_Z$  across it (thus across  $R_L$ )

$$I_{Z(\text{min})} = I_{Z(\text{knee})} = 3 \text{ mA} \quad (\text{Minimum current needed through zener})$$

$$I_{Z(\text{max})} = \frac{P_{Z(\text{max})}}{V_Z} = \frac{330 \text{ mW}}{3.3 \text{ V}} = 100 \text{ mA} \quad (\text{maximum allowable current through zener})$$

Maximum current passes through zener when  $I_S$  is maximum (i.e., when  $V_{in}$  is maximum) and  $I_L$  is minimum.  
& also  $R_S$  is minimum)

$$\begin{aligned} \therefore \text{Maximum current through zener diode} &= I_S(\text{max}) - I_L(\text{min}) = I_S(\text{max}) \\ &= \frac{V_{in}(\text{max}) - V_Z}{R_S(\text{min})} - \frac{V_Z}{R_L(\text{max})} \end{aligned}$$

This maximum current through the zener diode should be less than the maximum allowable current ( $I_z(\max)$ )

$$\therefore \frac{V_{in(\max)} - V_Z}{R_S(\min)} - \frac{V_Z}{R_L(\max)} < I_z(\max)$$

$$\Rightarrow \frac{25 - 3.3}{R_S(\min)} - \frac{3.3}{2k} < 100 \text{ mA}$$

$$\Rightarrow \frac{21.7}{R_S(\min)} < 101.65 \text{ mA}$$

$$\Rightarrow R_S(\min) > \frac{21.7}{101.65} \text{ k}\Omega \approx 215.52$$

$$R_S(\min) > 215.52$$

Minimum current passes through zener diode when  $I_S$  is minimum (i.e.,  $V_{in}$  is minimum and  $R_S$  is maximum) and  $I_L$  is maximum

$$\therefore \text{Minimum current through zener diode} = I_S(\min) - I_L(\max)$$

$$= \frac{V_{in(\min)} - V_Z}{R_S(\max)} - \frac{V_Z}{R_L(\min)}$$

This minimum current should be more than the knee current of the zener i.e.,  $I_z(\text{knee}) = I_z(\min)$

$$\therefore \frac{V_{in(\min)} - V_Z}{R_S(\max)} - \frac{V_Z}{R_L(\min)} > I_z(\min)$$

$$\Rightarrow \frac{20 - 3.3}{R_S(\max)} - \frac{3.3}{500} > 3 \text{ mA}$$

$$\Rightarrow \frac{16.7}{R_S(\max)} > 9.6 \text{ mA} \Rightarrow R_S(\max) < \frac{16.7}{9.6} \text{ k}\Omega \approx 1.74 \text{ k}\Omega$$

$$R_S(\max) < 1.74 \text{ k}\Omega$$

$\therefore$  Acceptable value of  $R_S$  should lie between  $215.52$  and  $1.74 \text{ k}\Omega$   
So we can choose  $R_S = 1 \text{ k}\Omega$  for proper operation of the regulator

$$215.52 < R_S < 1.74 \text{ k}\Omega$$

(Q5) The circuit shown in Fig. Q5 is an adjustable voltage regulator. Assume that the op-amp is ideal.

The zener ratings are as given below.

$I_Z(\text{knee}) = 0.01 \text{ mA}$  and  $P_Z(\text{max}) = 0.1 \text{ W}$ , and  $V_Z = 5\text{V}$ .

Design the value of  $R_S$  for proper operation of the zener diode. Also calculate the output voltage as  $R_2$  is varied from 0 to  $1\text{k}\Omega$ .  $V_S$  varies from 6V to 10V.

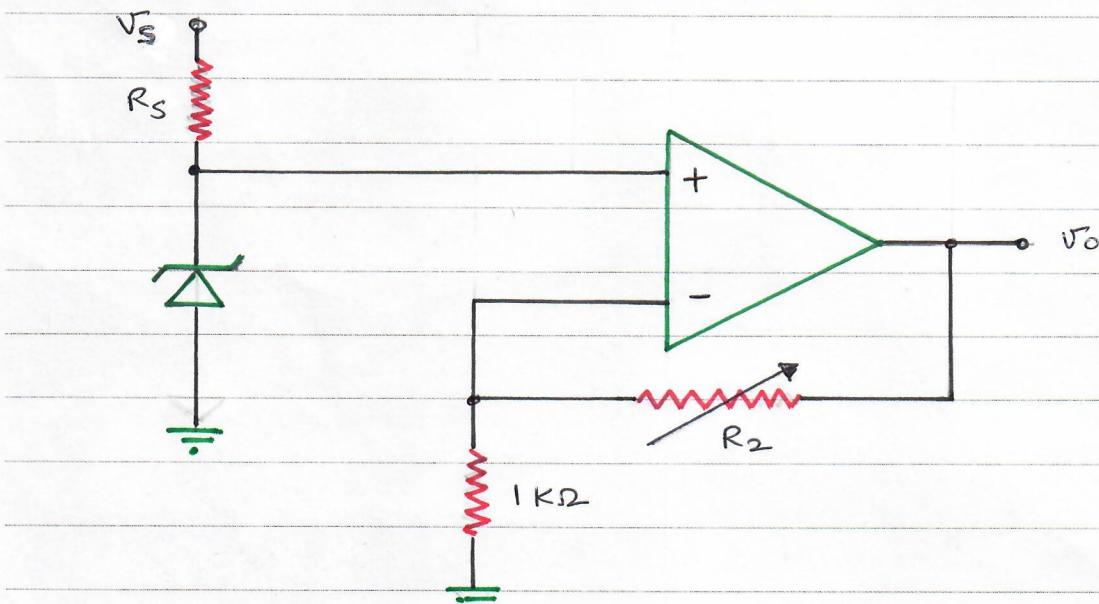


Fig. Q5

Sol.

$$I_Z = \frac{V_i - V_Z}{R_S}$$

$$I_Z(\text{max}) = \frac{V_i(\text{max}) - V_Z}{R_S(\text{min})} < \frac{P_Z(\text{max})}{V_Z}$$

$$\Rightarrow \frac{10 - 5}{R_S(\text{min})} < \frac{0.01}{5}$$

$$\Rightarrow \frac{5}{R_S(\text{min})} < 0.02$$

$$\Rightarrow R_S(\text{min}) > \frac{5}{0.02} = 250\Omega$$

$$I_z(\text{min}) = \frac{V_i(\text{min}) - V_z}{R_s(\text{max})} > 0.01 \times 10^{-3}$$

$$\Rightarrow \frac{6 - 5}{R_s(\text{max})} > 0.01 \times 10^{-3}$$

$$\Rightarrow R_s(\text{max}) < \frac{1}{10^{-5}} = 10^5 = 100 \text{ k}\Omega$$

$$\therefore 250\Omega < R_s < 100 \text{ k}\Omega$$

So, I can choose an  $R_s$  of  $1\text{ k}\Omega$  for proper operation of zener in the break down region.

$$V_o = V_z \times \left(1 + \frac{R_2}{1\text{ k}\Omega}\right)$$

$$= \left(1 + \frac{R_2}{1\text{ k}\Omega}\right) \times 5$$

$$R_2 \rightarrow 0 \text{ to } 1\text{ k}\Omega$$

$\therefore V_o$  can vary between 5 to 10V.

So, we can have an adjustable regulated voltage of 5 to 10V at the output pin of op-amp.