

Solutions to Tutorial Sheet - 4

IEC103

(Q1) Find the output voltage  $V_o$  of the amplifier circuit shown in Fig. Q1. Assume that all op-amps are ideal and none of the op-amps saturate.


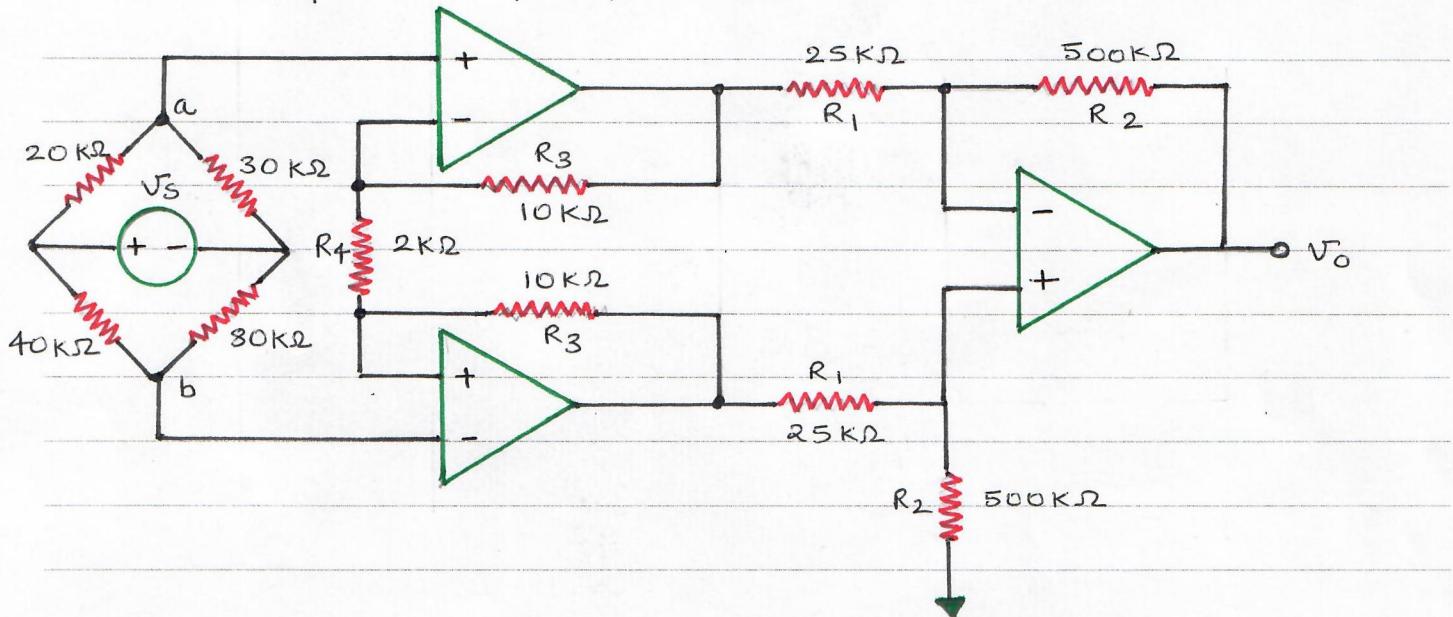


Fig. Q1

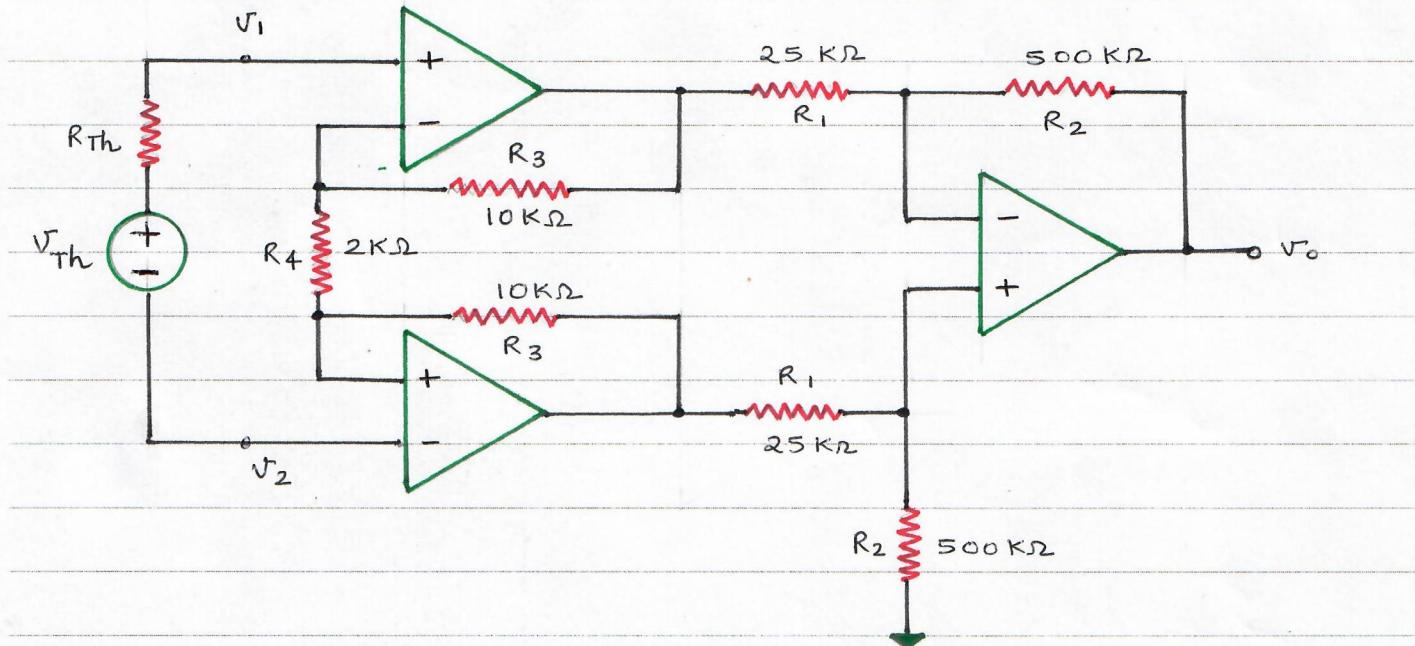Sol. Thevenizing bridge circuit across a-b.



$$R_{Th} = 20\text{ k}\Omega \parallel 30\text{ k}\Omega + 40\text{ k}\Omega \parallel 80\text{ k}\Omega$$

$$= \frac{20 \times 30}{50} + \frac{40 \times 80}{120} \text{ k}\Omega$$

$$= \frac{60}{5} + \frac{80}{3} \text{ k}\Omega = \frac{116}{3} \text{ k}\Omega$$

$$V_{th} = V_1 - V_2 = \frac{30}{30+20} V_S - \frac{80}{80+40} V_S$$

(current flows through  
the 1st stage  
(op-amps))

$$= \frac{30}{50} V_S - \frac{80}{120} V_S$$

$$= \frac{3}{5} V_S - \frac{8}{12} V_S = \frac{3}{5} V_S - \frac{2}{3} V_S$$

$$= -\frac{1}{15} V_S = V_1 - V_2$$

$$V_o = \left( \frac{R_2}{R_1} \right) \left( 1 + \frac{2R_3}{R_4} \right) (V_2 - V_1)$$

$$= \left( \frac{500K}{25K} \right) \left( 1 + \frac{2 \times 10K}{2K} \right) \times \frac{V_S}{15} \quad \therefore V_2 - V_1 = \frac{V_S}{15}$$

$$= 20 \times 11 \times \frac{V_S}{15} = \frac{220}{15} V_S = \frac{44}{3} V_S = 14.667 V_S$$

(Q2) The opamp circuit shown in Fig. Q2 is designed to amplify a voltage signal and current signal from two transducers. Applying superposition, find the output voltage  $V_o(t)$  in terms of inputs  $V_{IN}(t)$  and  $i_{IN}(t)$ . You may find it convenient to first find the  $\Delta$  values of intermediate variables  $V_1(t)$  and  $V_2(t)$  shown in the Fig. 2 and then find  $V_o(t)$ . Assume that opamps are ideal.


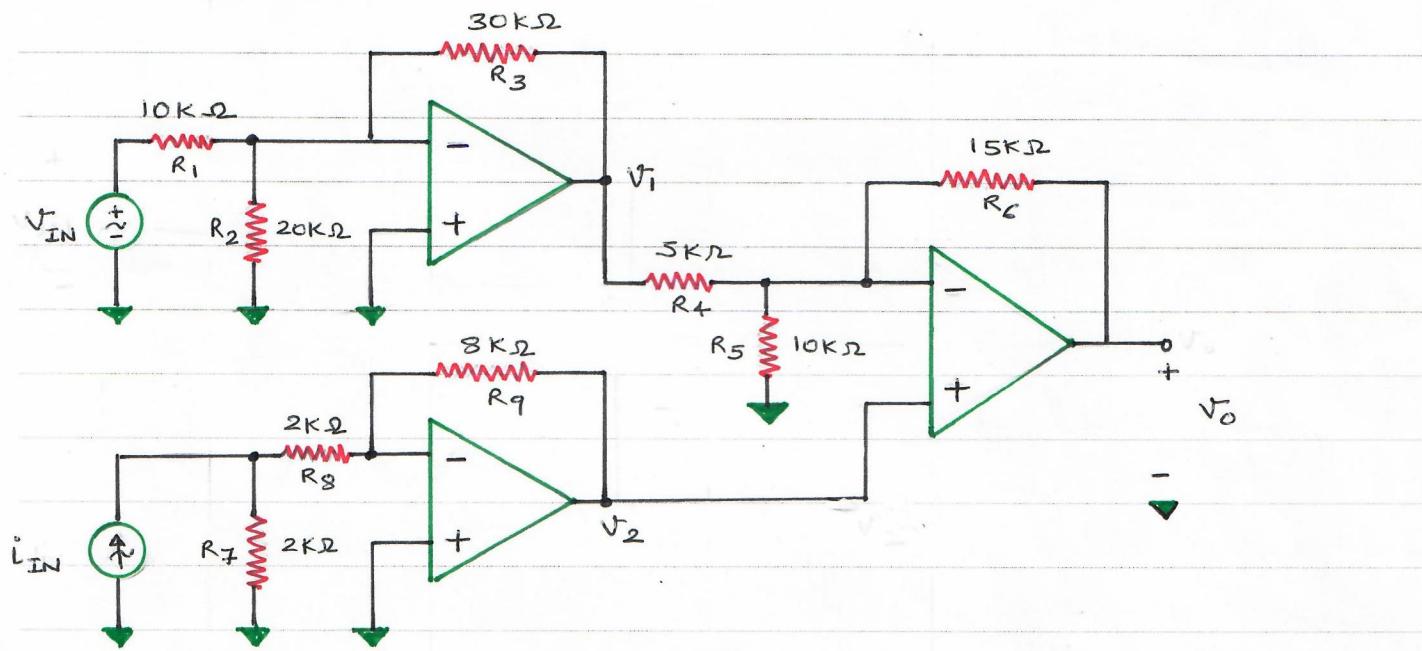



Fig. Q2

Sol.

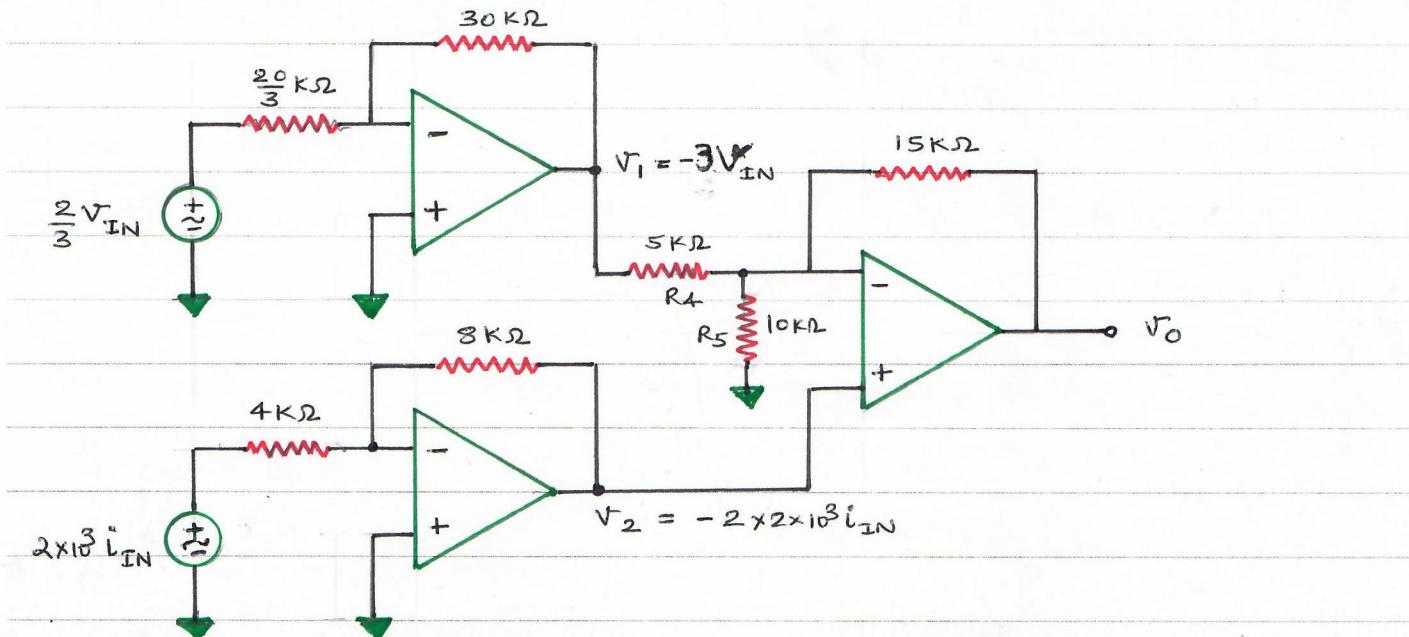
Using the Thevenin equivalent of source-1,  $V_{IN}$  along with  $R_1$  &  $R_2$  & source-2,  $i_{IN}$  along with  $R_7$ ,  $R_8$ .



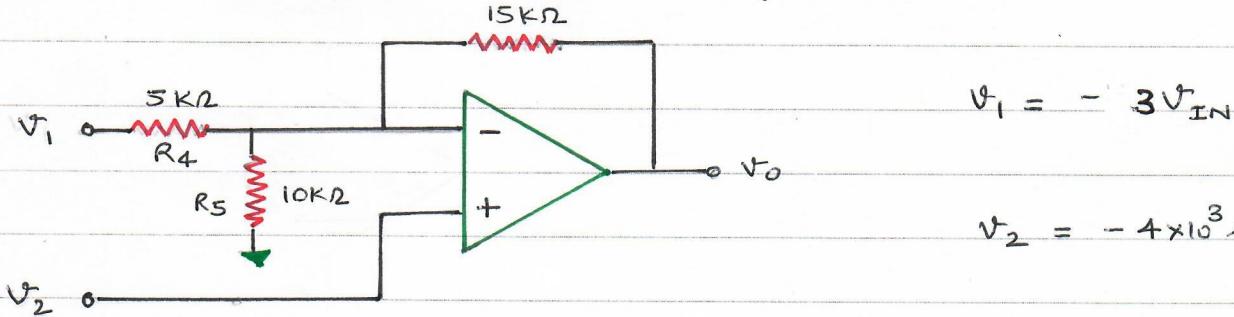Using Thevenin equivalent of  $V_1$  along with  $R_4, R_5$



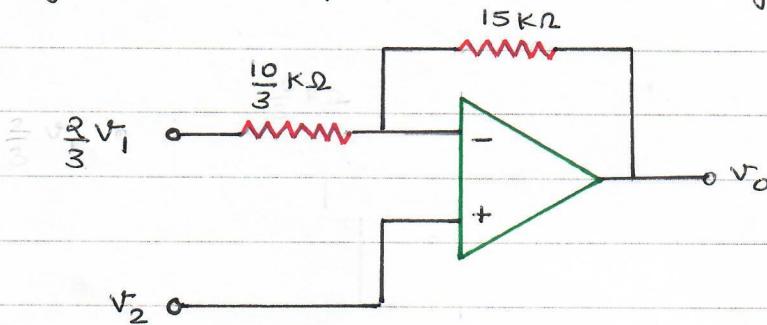Using Thevenin equivalent of  $V_1$  along with  $R_4, R_5$ .



$$V_0 = \left( \frac{-15K}{\left(\frac{10}{3}\right)K} \right) \times \frac{2}{3} V_1 + \left( 1 + \frac{15}{\left(\frac{10}{3}\right)} \right) V_2$$

$$= -\frac{45}{10} \times \frac{2}{3} V_1 + \left( 1 + \frac{45}{10} \right) V_2$$

$$= -3V_1 + 5.5V_2$$

$$= -3 \times -3V_{IN} + 5.5 \times -4 \times 10^3 i_{IN}$$

$$\Rightarrow \boxed{V_0 = 9V_{IN} - 22 \times 10^3 i_{IN}}$$

- (Q3) i) What type of feedback is incorporated in Q.3a, Q.3b, Q.3c, and Q.3d.  
ii) Assuming ideal op-amp, find  $\beta$  and  $A_f$  relevant to each circuit.

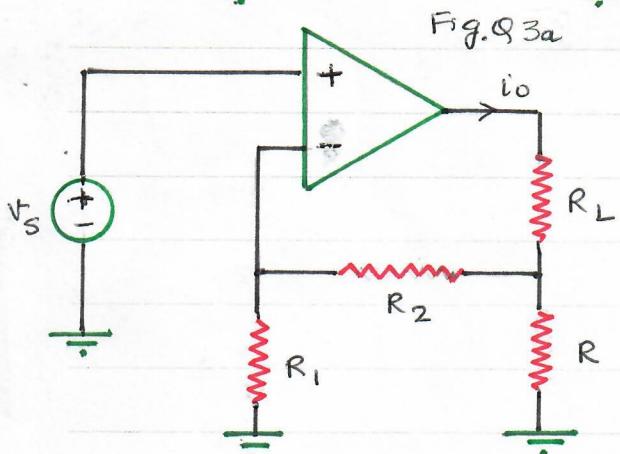
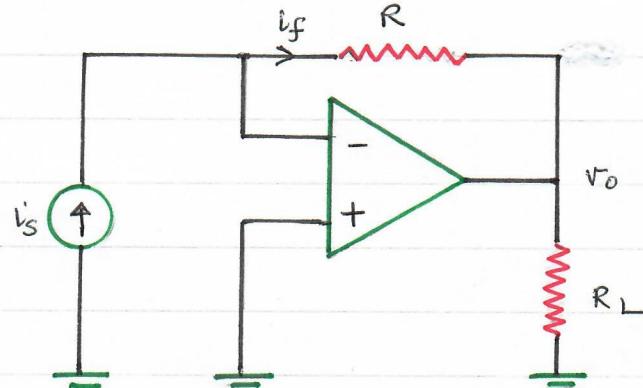
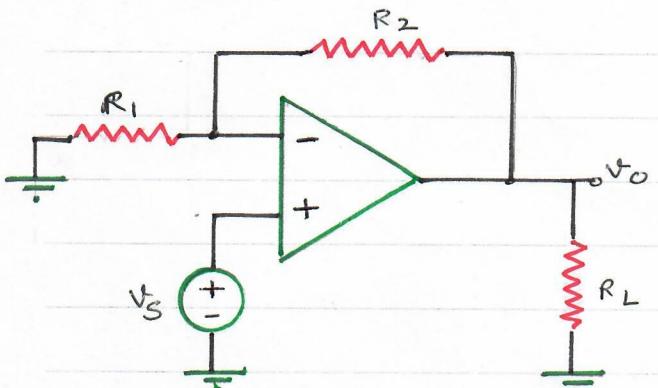


Fig. Q.3c

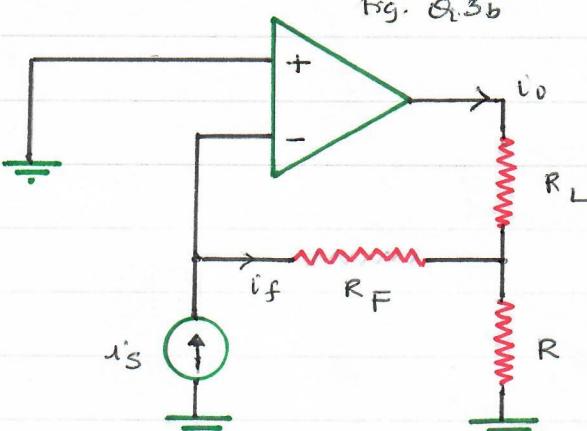


Fig. Q.3d

Sol.

a) Series - shunt configuration  
 $\uparrow$        $\nwarrow$   
(voltage mix) - (voltage sense)

$$\beta = \frac{V_F}{V_O} = \frac{R_1}{R_1 + R_2}$$

$$A_f = \frac{A}{1 + AB} = \frac{1}{\beta} \quad (\because A = \infty \text{ for ideal op-amp})$$

$$= \frac{1}{\left(\frac{R_1}{R_1 + R_2}\right)} = \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1}$$

$$A_f = 1 + \frac{R_2}{R_1} = \frac{V_O}{V_S}$$

b) Shunt - shunt configuration  
 ↓  
 (current mixing) → (voltage sense)

$$\beta = \frac{V_f}{V_o} = -\frac{(V_o/R)}{V_o} = -\frac{1}{R}$$

$$A_f = \frac{V_o}{i_s} = \frac{A}{1 + A\beta} = \frac{1}{\beta} \quad (\because A = \infty)$$

$$= \frac{1}{(1/R)} = -R$$

$$\therefore A_f = \frac{V_o}{i_s} = -R$$

c) Series - series configuration  
 ↓  
 (voltage mix) → (current sense)

$$\beta = \frac{V_f}{i_o} = \frac{i_o R' \times \frac{R_1}{(R_1+R_2)}}{i_o} \approx \frac{R R_1}{(R_1+R_2)}$$

$$R' = R \parallel (R_1+R_2) \approx R \quad \because R_1, R_2 \gg R$$

$$A_f = \frac{i_o}{V_s} = \frac{A}{1 + A\beta} = \frac{1}{\beta} \quad (\because A = \infty)$$

(assuming the  $R_1, R_2$   
 network does not  
 load o/p network  
 $(R_L - R)$ )

$$\Rightarrow A_f = \frac{R_1 + R_2}{R R_1} = \frac{1}{R} \left( 1 + \frac{R_2}{R_1} \right)$$

d) shunt - series configuration  
 ↴  
 (current mix) ↓ current sense

$$\beta = \frac{i_f}{i_o} = -\frac{i_o \times \left( \frac{R}{R_F+R} \right)}{i_o} = -\frac{R}{R_F+R}$$

$$A_f = \frac{i_o}{i_s} = \frac{A}{1 + A\beta} = \frac{1}{\beta} = \frac{1}{-\left(\frac{R}{R_F+R}\right)} = -\frac{R_F+R}{R} = -\left(1 + \frac{R_F}{R}\right)$$

$$\therefore A_f = \frac{i_o}{V_s} = -\left(1 + \frac{R_F}{R}\right)$$

Q4 For the amplifier circuit shown in Fig. Q4, find the expression for  $i_L$  in terms of  $V_S$ , if  $R_2 = R_4$  and  $R_1 = R_3$ . What type of amplifier is it?

Assume that the op-amp is ideal and operate in linear region.


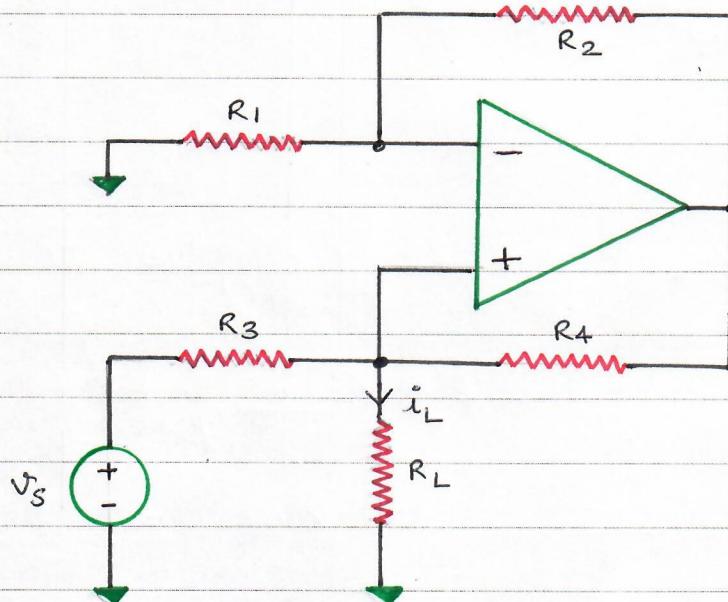


Fig. Q4

Sol.

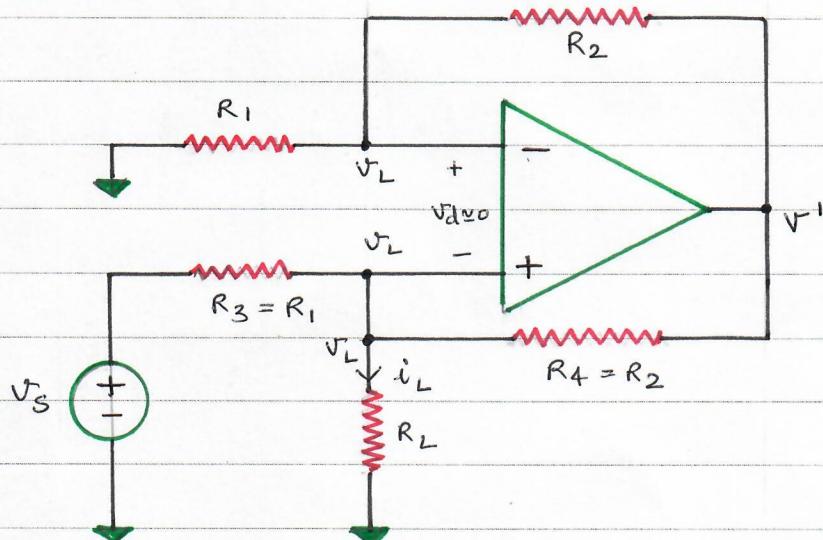

Applying KCL at non-inverting input of op-amp

$$\frac{V_L - V_S}{R_1} + \frac{V_L}{R_L} + \frac{V_L - V^+}{R_2} = 0 \quad \dots (A)$$

Applying KCL at inverting input of op-amp

$$\frac{V_L}{R_1} + \frac{V_L - V^I}{R_2} = 0$$

$$\Rightarrow V_L \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V^I}{R_2}$$

$$\Rightarrow V^I = R_2 \times V_L \frac{(R_1 + R_2)}{R_1 R_2}$$

$$\Rightarrow V^I = \frac{(R_1 + R_2) V_L}{R_1} \dots (B)$$

Substituting the expression for  $V^I$  in (B) in eq. (A)

Eq (A)

$$\frac{V_L - V_S}{R_1} + \frac{V_L}{R_L} + \frac{V_L - V^I}{R_2} = 0$$

$$\Rightarrow \frac{V_L - V_S}{R_1} + \frac{V_L}{R_L} + \left( V_L \left( \frac{1}{R_1} + \frac{1}{R_L} + \frac{1}{R_2} \right) - \frac{V^I}{R_2} \right) = \frac{V_S}{R_1}$$

$$\Rightarrow V_L \left( \frac{1}{R_1} + \frac{1}{R_L} + \frac{1}{R_2} \right) - (R_1 + R_2) V_L = \frac{V_S}{R_1}$$

$$\Rightarrow V_L \left( \frac{1}{R_1} + \frac{1}{R_L} + \frac{1}{R_2} \right) - \left( \frac{1}{R_1} + \frac{1}{R_2} \right) V_L = \frac{V_S}{R_1}$$

$$\Rightarrow \frac{V_L}{R_L} = \frac{V_S}{R_1}$$

$$\Rightarrow \frac{i_L R_L}{R_L} = \frac{V_S}{R_1}$$

$$\Rightarrow i_L = \frac{V_S}{R_1}$$

Load current depends on source (input) voltage irrespective of load resistance ( $R_L$ ). It is a transconductance amplifier.

(Q5) Fig. Q5 shows a feedback transconductance amplifier implemented using an op amp with open-loop gain  $A_{OL}$ , a very large input resistance, and an output resistance  $r_o$ . The output current  $I_o$  that is delivered to the load resistance  $R_L$  is sensed by the feedback network composed of three resistances  $R_M$ ,  $R_1$ , and  $R_2$ , and a proportional voltage  $V_f$  is fed back to the negative-input terminal of the op amp. Find the expressions for  $A = I_o/V_s$ ,  $\beta = V_f/I_o$ , and  $A_f = I_o/V_s$ . If the loop gain is large, find the approximate expression for  $A_f$  (closed-loop gain).


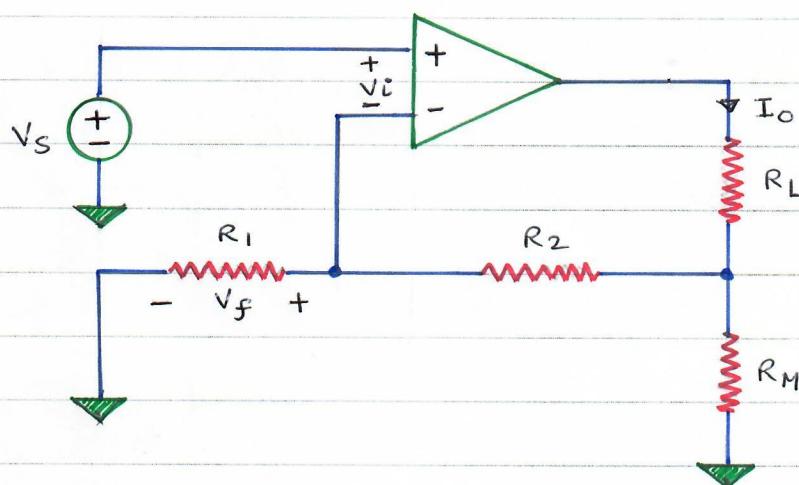


Fig. Q5

Sol.

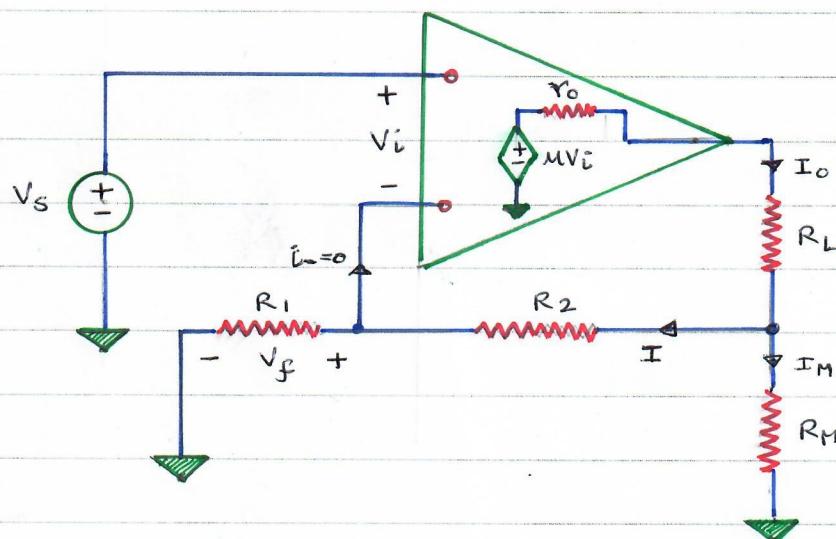Replacing op-amp by its equivalent circuit



$$a) A = G_M = I_0 / V_i$$

$$M V_C = r_o I_0 + R_L I_0 + R_M I_M$$

$$M V_i = r_o I_0 + I_0 R_L + \frac{I_0 \times (R_1 + R_2)}{(R_1 + R_2) + R_M} \times R_M$$

$$\Rightarrow M V_i = \left[ r_o + R_L + \frac{R_M (R_1 + R_2)}{(R_1 + R_2) + R_M} \right] I_0$$

$$\Rightarrow A = \frac{I_0}{V_i} = \frac{\mu}{r_o + R_L + \frac{R_M (R_1 + R_2)}{(R_1 + R_2) + R_M}}$$

$$b) \beta = V_f / I_0$$

$$V_f = R_1 I \\ = R_1 \times \frac{R_M}{(R_1 + R_2) + R_M} \times I_0$$

$$\Rightarrow V_f = \frac{R_1 R_M}{(R_1 + R_2) + R_M} I_0$$

$$\Rightarrow \beta = \frac{V_f}{I_0} = \frac{R_1 R_M}{(R_1 + R_2) + R_M}$$

$$c) A_f = I_0 / V_s$$

$$V_s = V_f + V_i \\ = \frac{R_1 R_M}{(R_1 + R_2) + R_M} \times I_0 + \frac{I_0}{A}$$

$$\Rightarrow V_s = \left[ \frac{R_1 R_M}{(R_1 + R_2) + R_M} + \frac{1}{A} \right] I_0$$

$$\Rightarrow \frac{I_0}{V_s} = \frac{1}{\left[ \frac{R_1 R_M}{(R_1 + R_2) + R_M} + \frac{1}{A} \right]}$$

$$\Rightarrow A_f = \frac{1}{\left[ \frac{R_1 R_M}{(R_1 + R_2) + R_M} + \frac{1}{A} \left( r_o + R_L + \frac{R_M (R_1 + R_2)}{(R_1 + R_2) + R_M} \right) \right]}$$

Using feedback theory  $A_f = \frac{A}{1 + AB}$  where  $AB$  = loop gain

If  $AB$  is very large,  $1 + AB \approx AB$

$$\therefore A_f \approx \frac{A}{AB} = \frac{1}{B}$$

$$\therefore A_f (\text{with very high loop gain}) = \frac{1}{B} = \frac{(R_1 + R_2) + R_m}{R_1 R_m}$$